

# De-multiplexer

# Introduction

- A De-multiplexer is a combinational circuit that has only 1 input line and  $2^N$  output lines.
- Simply, the multiplexer is a single-input and multi-output combinational circuit.
- The information is received from the single input lines and directed to the output line.

- On the basis of the values of the selection lines, the input will be connected to one of these outputs.
- De-multiplexer is opposite to the multiplexer.
- Unlike encoder and decoder, there are  $n$  selection lines and  $2^n$  outputs. So, there is a total of  $2^n$  possible combinations of inputs.
- De-multiplexer is also treated as **De-mux**.


# Types

- There are various types of De-multiplexer which are as follows:

# 1×2 De-multiplexer:

- In the 1 to 2 De-multiplexer, there are only two outputs,
- i.e.,  $Y_0$ , and  $Y_1$ ,
- 1 selection lines, i.e.,  $S_0$ ,
- and single input, i.e.,  $A$ .
- On the basis of the selection value, the input will be connected to one of the outputs.
- The block diagram and the truth table of the 1×2 multiplexer are given below.

# Block Diagram:

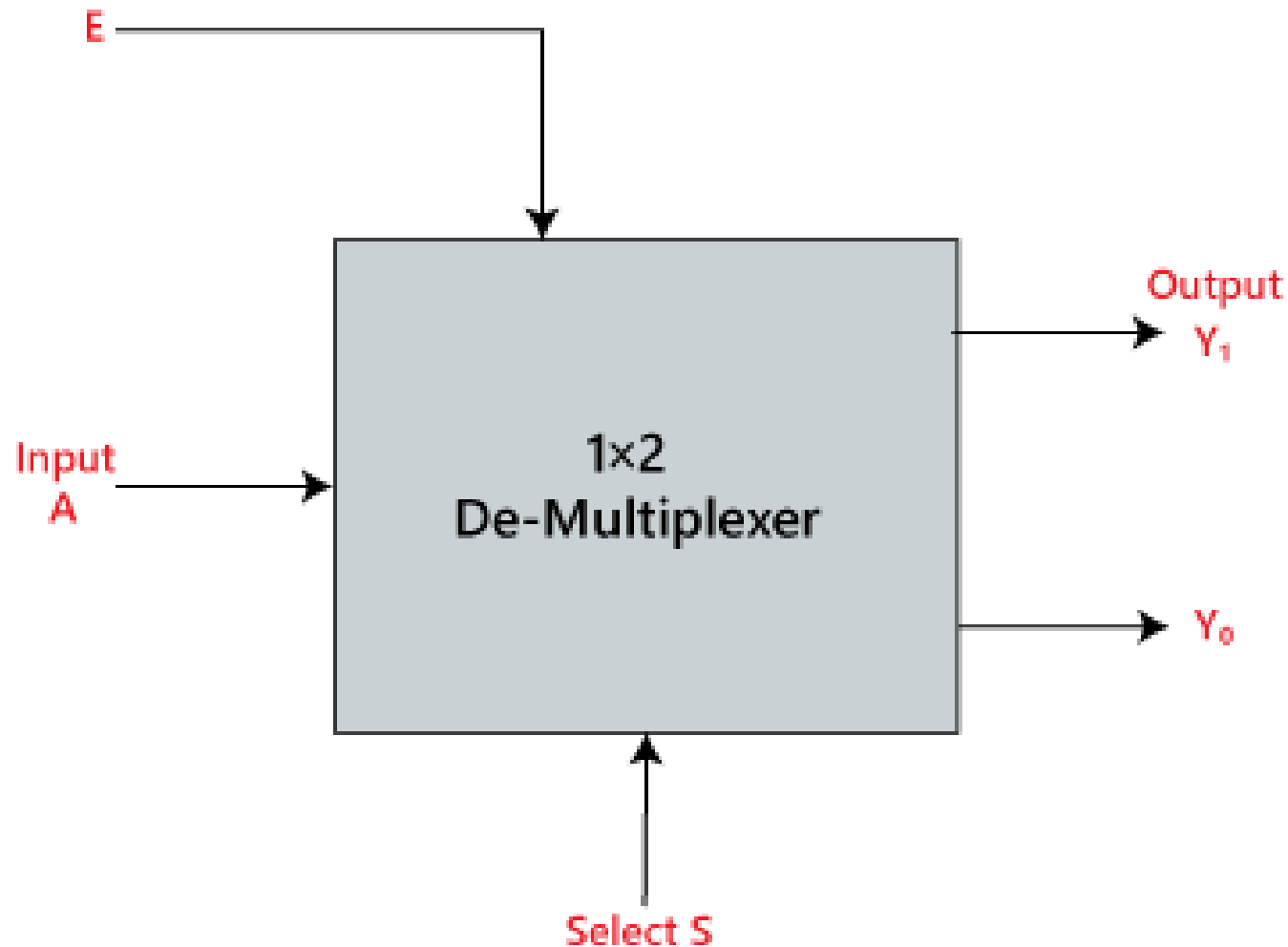

# Truth Table:


INPUTS	Output	
$S_0$	$Y_1$	$Y_0$
0	0	A
1	A	0

The logical expression of the term Y is as follows:

$$Y_0 = S_0' \cdot A$$

$$Y_1 = S_0 \cdot A$$

 Logical circuit of the above expressions is given below:






# 1×4 De-multiplexer:

- In 1 to 4 De-multiplexer, there are total of four outputs, i.e.,  $Y_0$ ,  $Y_1$ ,  $Y_2$ , and  $Y_3$ ,
- 2 selection lines, i.e.,  $S_0$  and  $S_1$
- and single input, i.e.,  $A$ .
- On the basis of the combination of inputs which are present at the selection lines  $S_0$  and  $S_1$ , the input be connected to one of the outputs.
- The block diagram and the truth table of the 1×4 multiplexer are given below.

# Block Diagram:

 


# Truth Table:

INPUTS		Output			
$S_1$	$S_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	A
0	1	0	0	A	0
1	0	0	A	0	0
1	1	A	0	0	0

- The logical expression of the term Y is as follows:
- $Y_0 = S_1' S_0' A$   
 $y_1 = S_1' S_0 A$   
 $y_2 = S_1 S_0' A$   
 $y_3 = S_1 S_0 A$

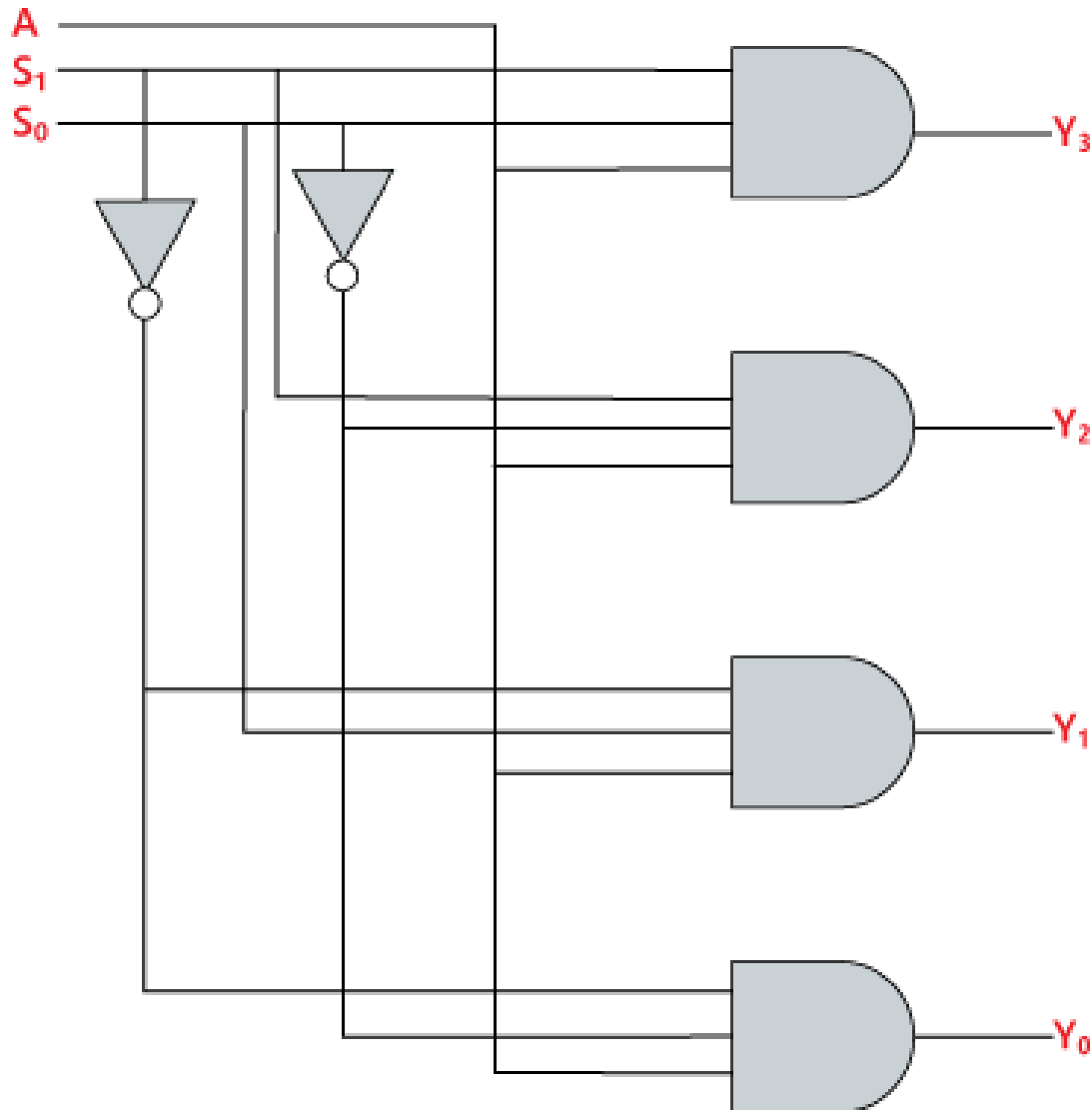
Logical circuit of the above expressions is given below:



# 1×8 De-multiplexer

- In 1 to 8 De-multiplexer, there are total of eight outputs, i.e.,  $Y_0$ ,  $Y_1$ ,  $Y_2$ ,  $Y_3$ ,  $Y_4$ ,  $Y_5$ ,  $Y_6$ , and  $Y_7$ ,
- 3 selection lines, i.e.,  $S_0$ ,  $S_1$  and  $S_2$
- and single input, i.e.,  $A$ .
- On the basis of the combination of inputs which are present at the selection lines  $S^0$ ,  $S^1$  and  $S_2$ , the input will be connected to one of these outputs.
- The block diagram and the truth table of the 1×8 de-multiplexer are given below.

# Block Diagram:

 

# Truth Table:


INPUTS			Output							
S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Y <sub>7</sub>	Y <sub>6</sub>	Y <sub>5</sub>	Y <sub>4</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	0	0	0	0	0	0	0	0	0	A
0	0	1	0	0	0	0	0	0	A	0
0	1	0	0	0	0	0	0	A	0	0
0	1	1	0	0	0	0	A	0	0	0
1	0	0	0	0	0	A	0	0	0	0
1	0	1	0	0	A	0	0	0	0	0
1	1	0	0	A	0	0	0	0	0	0
1	1	1	A	0	0	0	0	0	0	0



The logical expression of the term Y is as follows:

- $Y_0 = S_0' . S_1' . S_2' . A$   
 $Y_1 = S_0 . S_1' . S_2' . A$   
 $Y_2 = S_0' . S_1 . S_2' . A$   
 $Y_3 = S_0 . S_1 . S_2' . A$   
 $Y_4 = S_0' . S_1' . S_2 . A$   
 $Y_5 = S_0 . S_1' . S_2 . A$   
 $Y_6 = S_0' . S_1 . S_2 . A$   
 $Y_7 = S_0 . S_1 . S_3 . A$

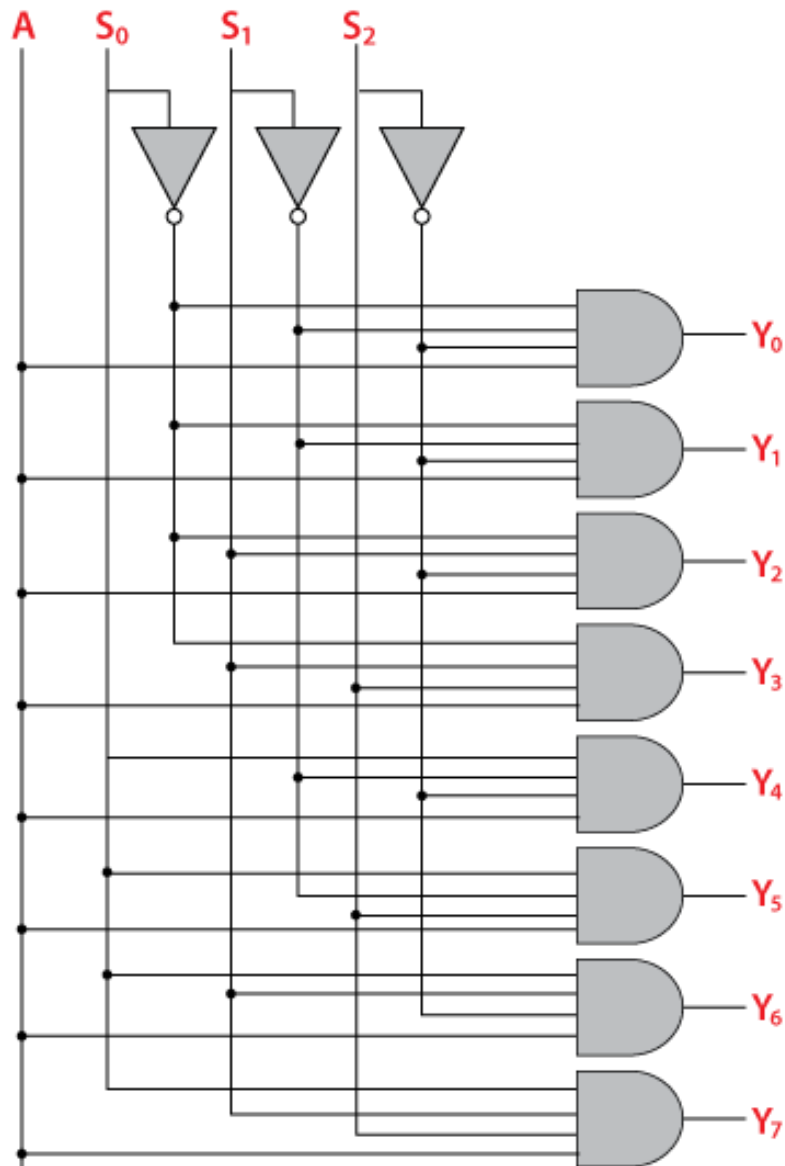
Logical circuit of the above expressions is given below:


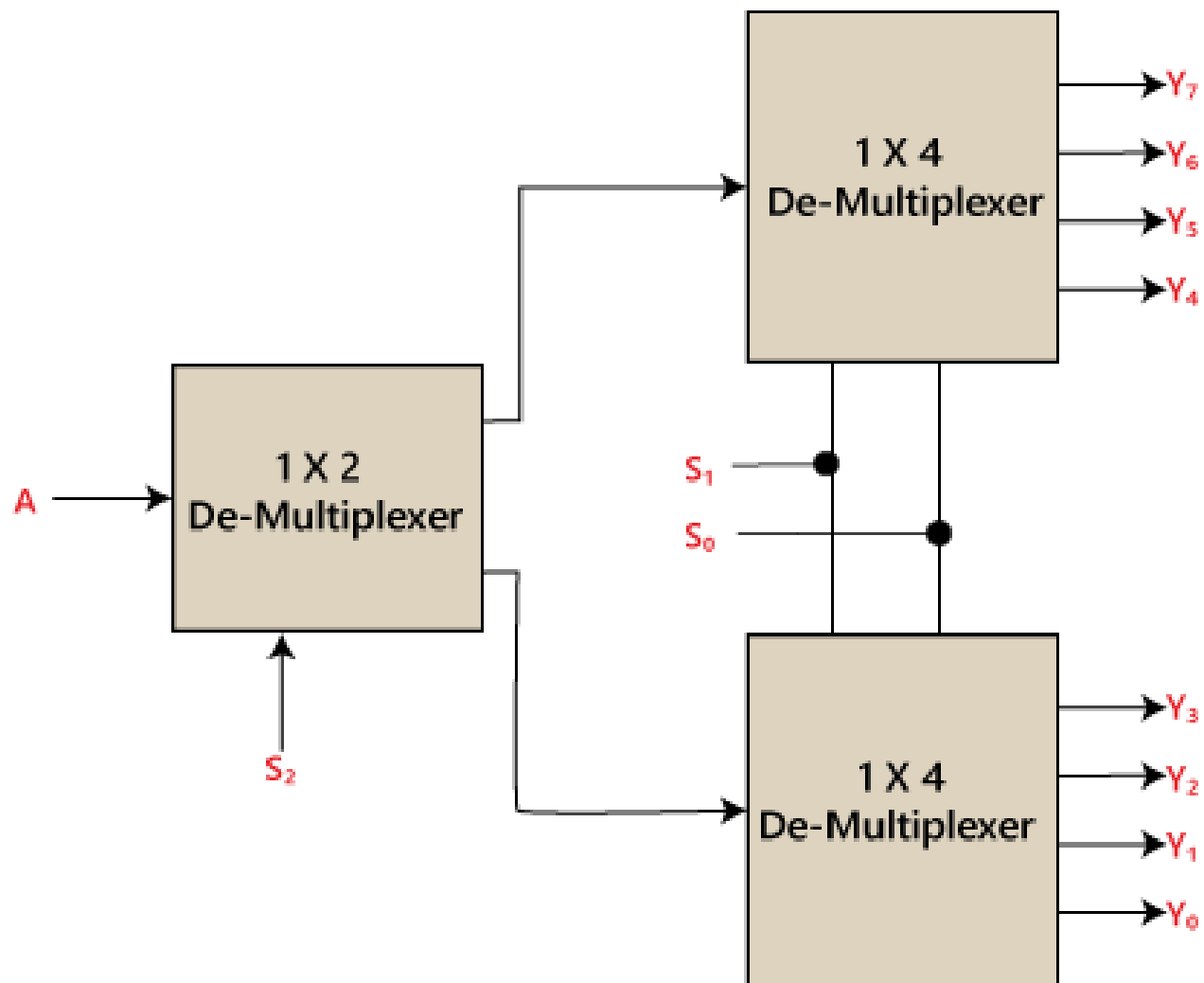
## 1×8 De-multiplexer using 1×4 and 1×2 de-multiplexer

- We can implement the 1×8 de-multiplexer using a lower order de-multiplexer.
- To implement the 1×8 de-multiplexer, we need two 1×4 de-multiplexer and one 1×2 de-multiplexer.
- The 1×4 multiplexer has 2 selection lines, 4 outputs, and 1 input.
- The 1×2 de-multiplexer has only 1 selection line.


- For getting 8 data outputs, we need two  $1 \times 4$  de-multiplexer.
- The  $1 \times 2$  de-multiplexer produces two outputs.
- So, in order to get the final output, we have to pass the outputs of  $1 \times 2$  de-multiplexer as an input of both the  $1 \times 4$  de-multiplexer.
- The block diagram of  $1 \times 8$  de-multiplexer using  $1 \times 4$  and  $1 \times 2$  de-multiplexer is given below.



# 1 x 16 De-multiplexer

- In 1×16 de-multiplexer, there are total of 16 outputs, i.e.,  $Y_0, Y_1, \dots, Y_{16}$ , 4 selection lines, i.e.,  $S_0, S_1, S_2$ , and  $S_3$  and single input, i.e.,  $A$ .
- On the basis of the combination of inputs which are present at the selection lines  $S^0, S^1$ , and  $S_2$ , the input will be connected to one of these outputs.
- The block diagram and the truth table of the 1×16 de-multiplexer are given below.

# Block diagram

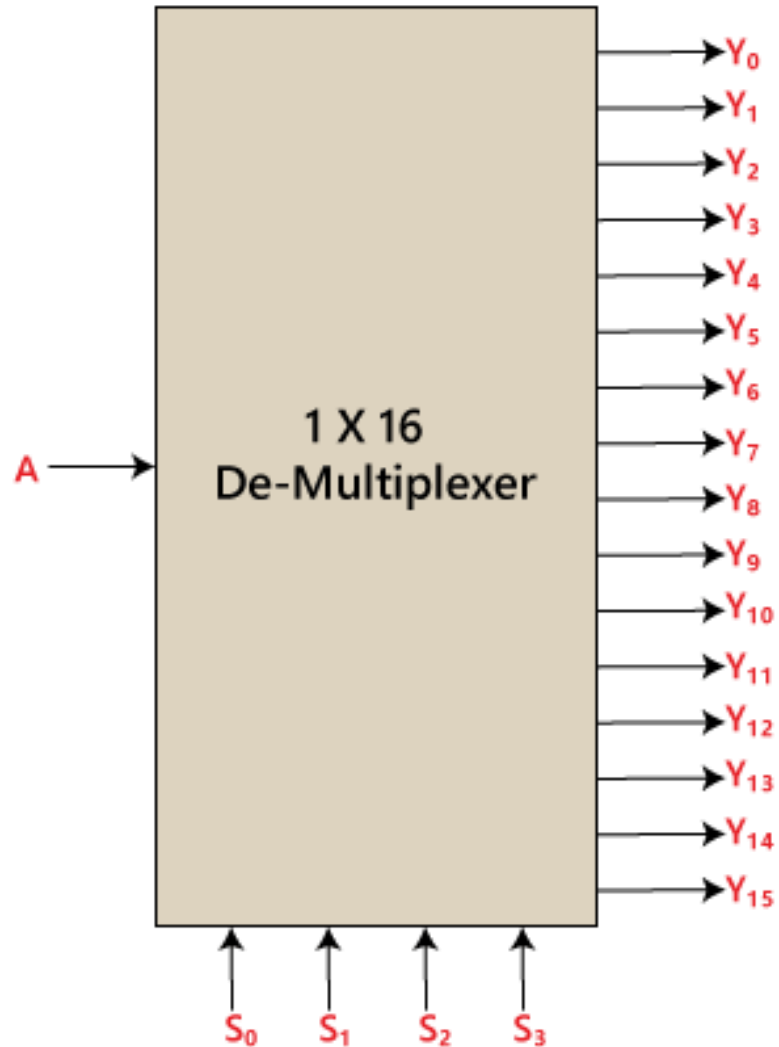

## Truth Table:

[illegible]





The logical expression of the term Y is as follows:

$$Y_0 = A.S_0'.S_1'.S_2'.S_3'$$

$$Y_1 = A.S_0'.S_1'.S_2'.S_3$$

$$Y_2 = A.S_0'.S_1'.S_2.S_3'$$

$$Y_3 = A.S_0'.S_1'.S_2.S_3$$

$$Y_4 = A.S_0'.S_1.S_2'.S_3'$$

$$Y_5 = A.S_0'.S_1.S_2'.S_3$$

$$Y_6 = A.S_0'.S_1.S_2.S_3'$$

$$Y_7 = A.S_0'.S_1.S_2.S_3$$

$$Y_8 = A.S_0.S_1'.S_2'.S_3'$$

$$Y_9 = A.S_0.S_1'.S_2'.S_3$$

$$Y_{10} = A.S_0.S_1'.S_2.S_3'$$

$$Y_{11} = A.S_0.S_1'.S_2.S_3$$


$$Y_{12} = A.S_0.S_1.S_2'.S_3'$$

$$Y_{13} = A.S_0.S_1.S_2'.S_3$$

$$Y_{14} = A.S_0.S_1.S_2.S_3'$$

$$Y_{15} = A.S_0.S_1.S_2'.S_3$$

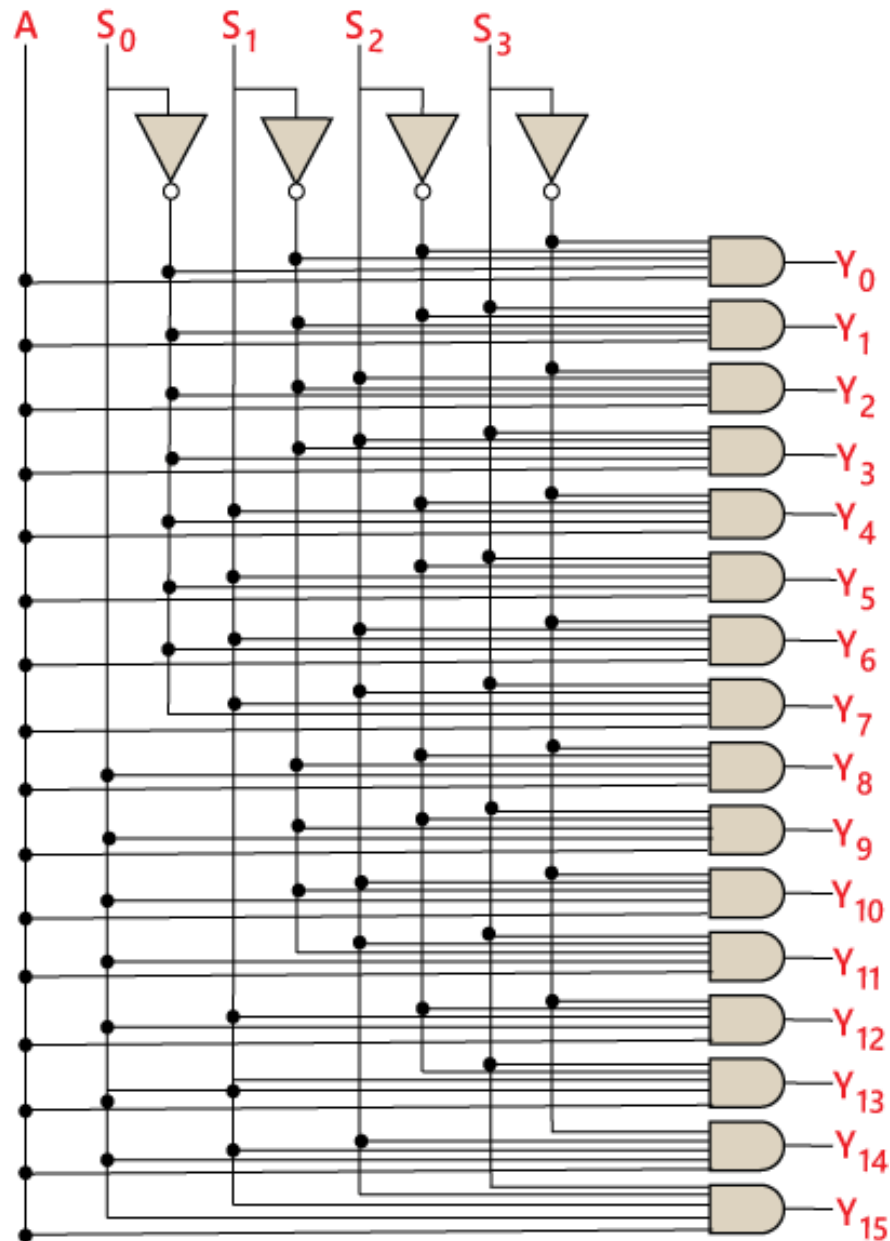Logical circuit of the above expressions is given below:



## 1×16 de-multiplexer using 1×8 and 1×2 de-multiplexer

- We can implement the 1×16 de-multiplexer using a lower order de-multiplexer.
- To implement the 1×16 de-multiplexer, we need two 1×8 de-multiplexer and one 1×2 de-multiplexer.
- The 1×8 multiplexer has 3 selection lines, 1 input, and 8 outputs.
- The 1×2 de-multiplexer has only 1 selection line.

- For getting 16 data outputs, we need two  $1 \times 8$  de-multiplexer.
- The  $1 \times 8$  de-multiplexer produces eight outputs. So, in order to get the final output, we need a  $1 \times 2$  de-multiplexer to produce two outputs from a single input.
- Then we pass these outputs into both the de-multiplexer as an input.
- The block diagram of  $1 \times 16$  de-multiplexer using  $1 \times 8$  and  $1 \times 2$  de-multiplexer is given below.

