
Decoder 74138

Decoder 74138

- IC 74138 is a Logical Decoder IC.
- It also has a demultiplexing facility.
- The IC 74138 is available in the market with the name of 74LS138.
- It is a 3 to 8 decoder IC.
- The internal circuit of this IC is made of highspeed Schottky barrier diode.


IC 74138 Pin Diagram

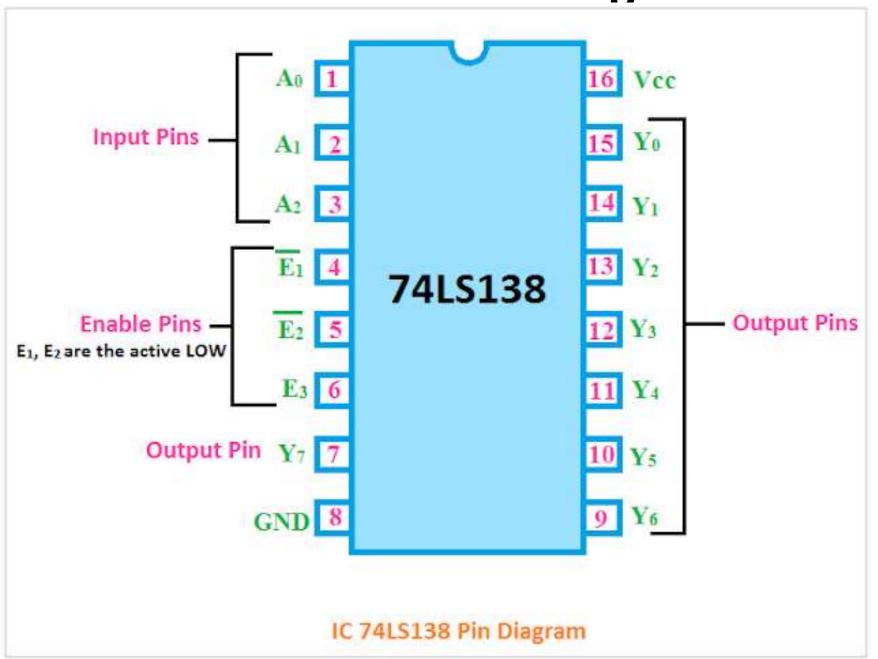

- 1. The pin no. 8 and 16 are the ground and Vcc respectively for the power input.
- 2. There are a total of three input pins(pin no. 1, 2, 3).
- They are denoted by A0, A1, A2.
- So the IC 74LS138 can take three binary input signals.

- 3. There are three enable input pins E1, E2, E3(pin no. 4, 5, 6).
- E1 and E2 are the active LOW pins that mean when low signals are applied to those pins they will be active.
- 4. Pin no. 7 and 9 to 15 are the output pins.

Logical Diagram of IC 74138

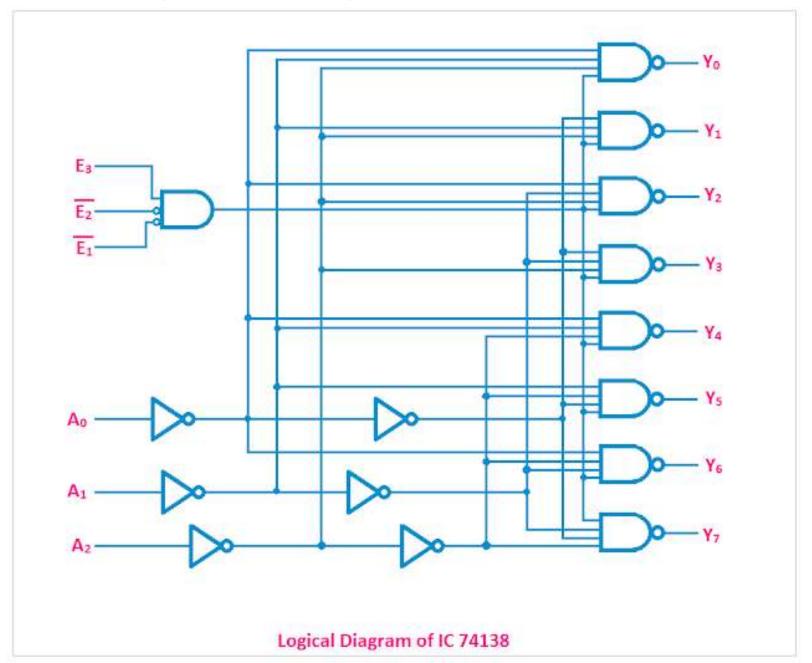

IC 74138 Truth Table

INPUTS						OUTPUTS							
E ₁	E ₂	E 3	A ₀	A ₁	A ₂	Y ₀	Υ ₁	Y ₂	Υ3	Υ4	Y 5	Y 6	Y 7
Н	Х	Х	Х	Х	Х	Н	Н	Н	Н	Н	Н	Н	Н
Х	Н	Χ	Х	Χ	Х	Н	Н	Н	Н	Н	Н	Н	Н
Х	Х	L	Х	Χ	Х	Н	Н	Н	Н	Н	Н	Н	Н
L	L	Н	L	L	L	L	Н	Н	Н	Н	Н	Н	Н
L	L	Н	Н	L	L	Н	L	Н	Н	Н	Н	Н	Н
L	L	Н	L	Н	L	Н	Н	L	Н	Н	Н	Н	Н
L	L	Н	Н	Н	L	Н	Н	Н	L	Н	Н	Н	Н
L	L	Н	L	L	Н	Н	Н	Н	Н	L	Н	Н	Н
L	L	Н	Н	L	Н	Н	Н	Н	Н	Н	L	Н	Н
L	L	Н	L	Н	Н	Н	Н	Н	Н	Н	Н	L	Н
L	L	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	L

H - High, L - Low, X - Don't Care

Operating Condition of IC 74138

- 1. The supply voltage or Vcc should be given between 4.75V to 5.25V
- 2. Operating temperature range should be between 0 to 70-degree centigrade

Features and Electrical characteristics of IC 74138

- It is very fast and high-speed IC.
- It consumes very low power because it consists of low power Schottky diodes (32mW).
- It has a de-multiplexing facility.
- Incorporates three enable pins to simplify cascading

- Inputs accept voltages higher than VCC
- Supply voltage: 1.0V to 5.5V
- Typical propagation delay: 21nS
- Low power consumption: 32mW
- Operating temperature: -40°C to +125°C


- ESD protection
- Protection against electrostatic discharges
 (ESD) is part of EMC Immunity (Electro
 Magnetic Compatibility) requirements. It
 is the ability for equipment to properly
 operate in its electromagnetic environment
 by limiting the reception of electromagnetic
 energy that may cause physical damage.

How to use 74LS138 Decoder

 For understanding the working of device let us construct a simple application circuit with a few external components as shown below.

IC 74138 Applications

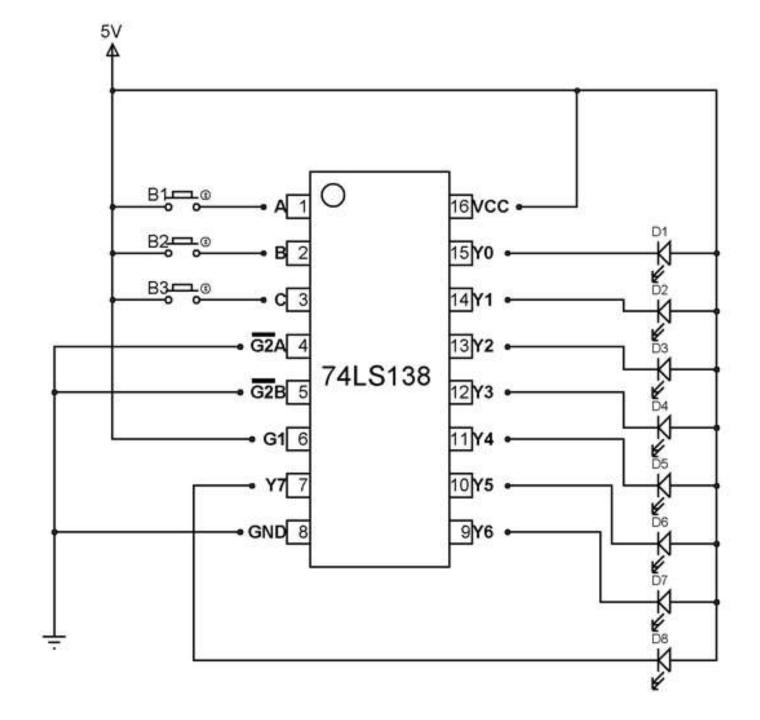- 1. Decode the digital signal.
- 2. digital memory circuits.
- 3. data routing applications.
- 4. de-multiplexing of digital signals.
- 5.Servers
- 6.Telecom circuits



- About circuit: Here the outputs are connected to LED to show which output pin goes LOW and do remember the outputs of the device are inverted.
- We are using a single device so we will connect G2A and G2B pin to ground followed by connecting G1 to VCC to enable the chip.
- The three buttons here represent three input lines for the device.

Implementing function using Decoder

Implement Boolean function $f = \Sigma m(1,2,3,7)$ using 3:8 decoder

