

 


Shift registers

 

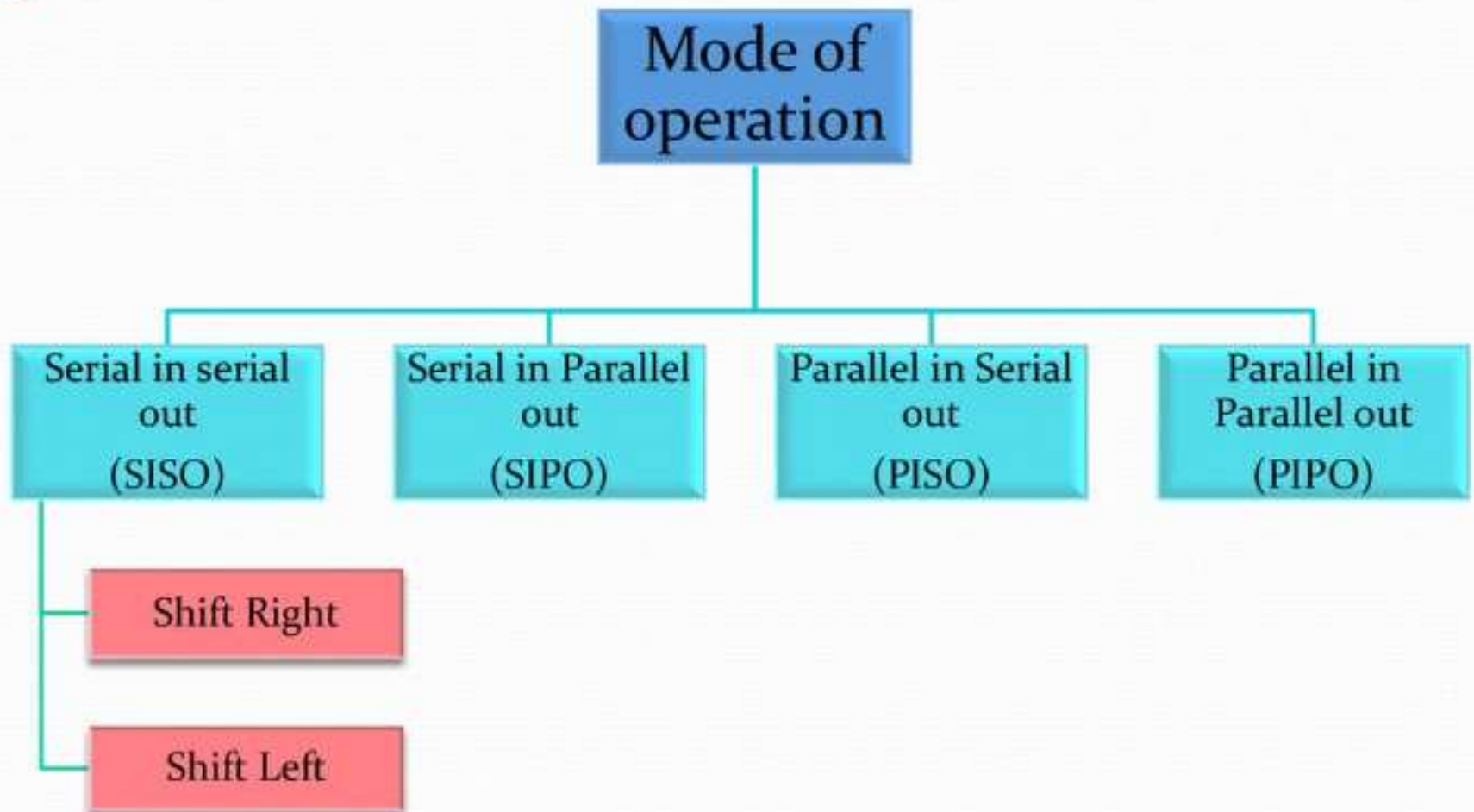

Classification of Registers :




COMBINATIONS OF DATA TRANSFER METHODS

- SISO: Serial In, Serial Out




- SIPO: Serial In, Parallel Out

 


COMBINATIONS OF DATA TRANSFER METHODS

- PISO: Parallel In, Serial Out

 


- PIPO: Parallel In, Parallel Out

 

Shift Register

Sr. No.	Mode	Illustrative Diagram	Comments
1.	SISO (Shift Right)		Data bits shift from Left to Right by 1 position per clock cycle.
2.	SISO (Shift Left)		Data bits shift from Right to Left by 1 position per clock cycle.
3.	SIPO		All o/p bits are made avail. simult. after 4-clcok pulse
4.	PISO		All i/p bits are applied simult and. After 4-clk pulse the required o/p is available serially.

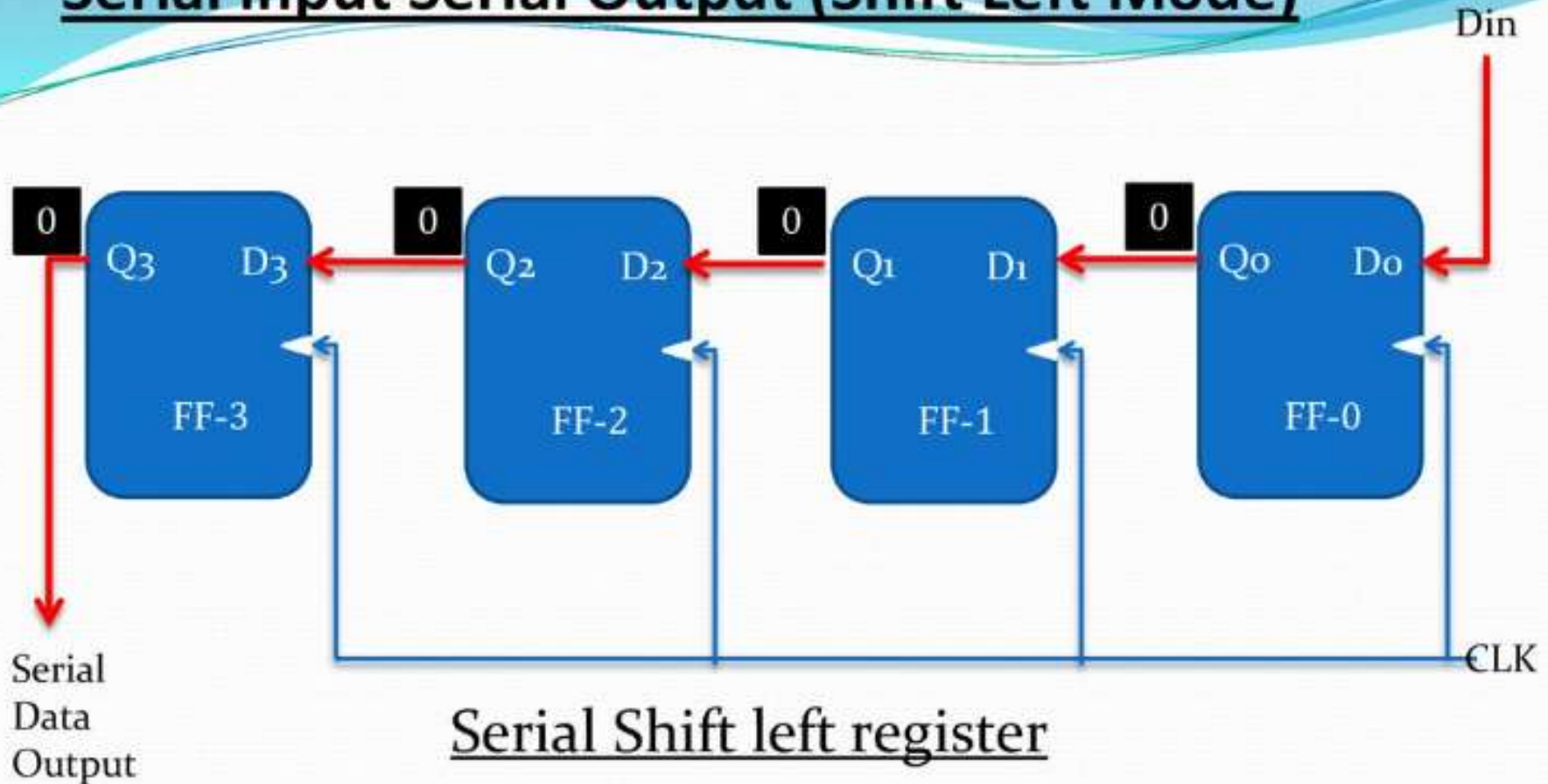Serial input Serial Output (Shift Left Mode)




- Before application of clock let assume all outputs are zero and apply MSB bit of the number to entered to Din. So Din = D₀ = 1.

Serial input Serial Output (Shift Left Mode)

- Apply the clock . On the first falling edge of clock, the FF-0 is SET and the stored data in the register is


$$Q_3Q_2Q_1Q_0 = 0\ 0\ 0\ 1$$

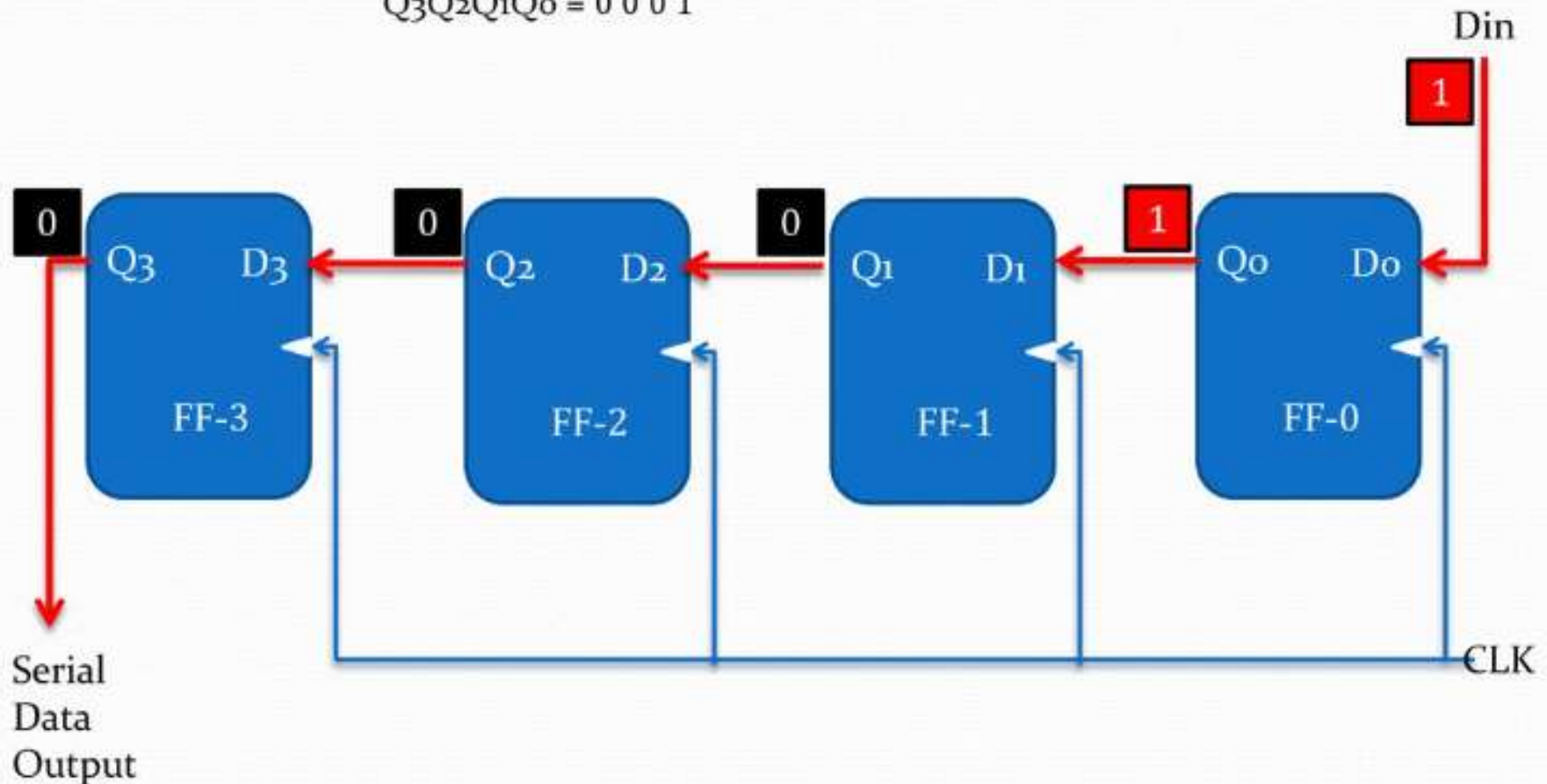

Serial input Serial Output (Shift Left Mode)

- Apply the NEXT bit to Din . So if Din =1.
- As soon as the next positive edge of the clock hits. FF- 1 will SET and the stored data changes to,


$Q_3Q_2Q_1Q_0 = 0\ 0\ 1\ 1$

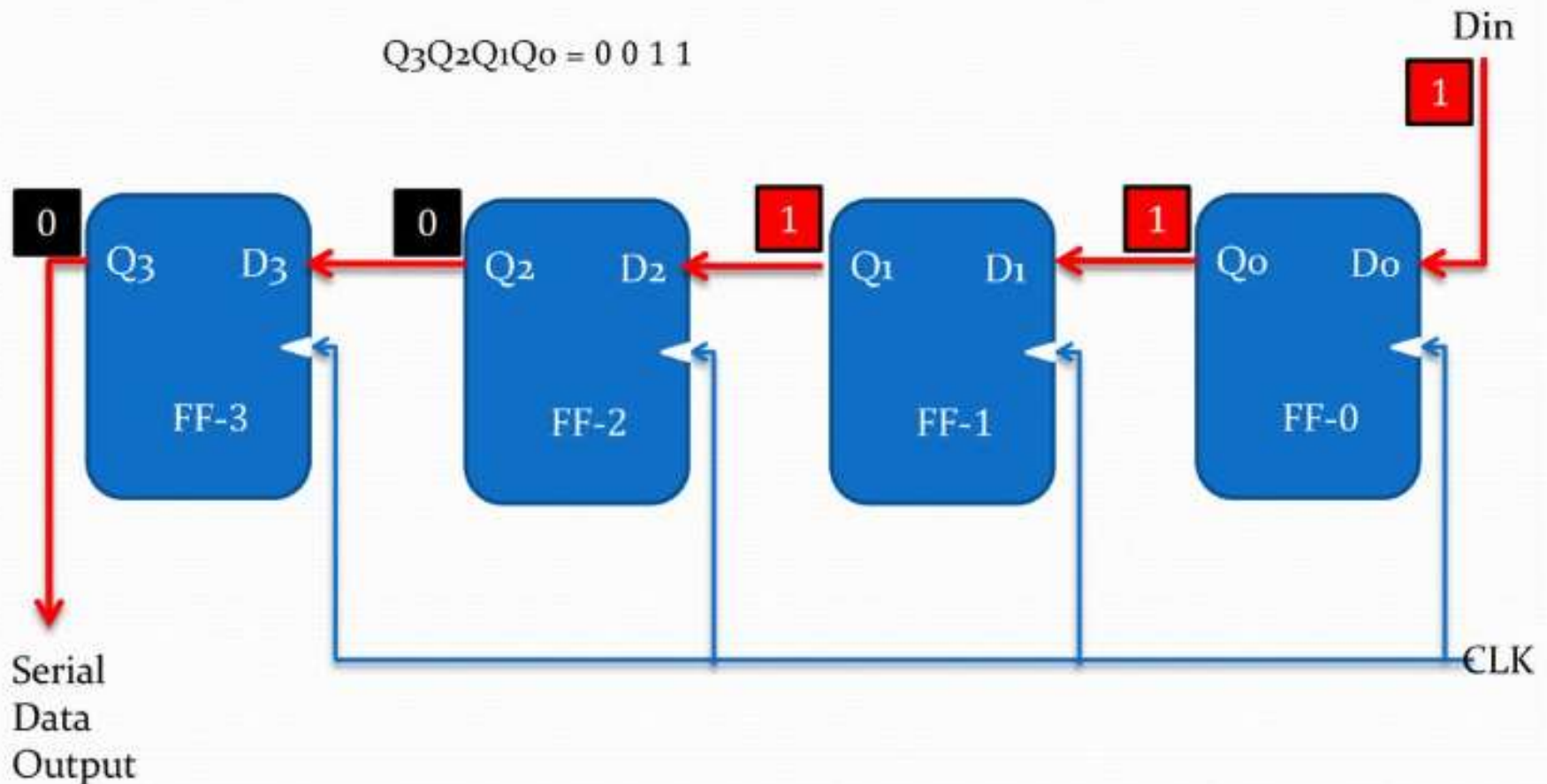

Serial input Serial Output (Shift Left Mode)

- Apply the NEXT bit to Din . So if Din =1.
- As soon as the next positive edge of the clock hits. FF- 2will SET and the stored data changes to,


$Q_3Q_2Q_1Q_0 = 0111$

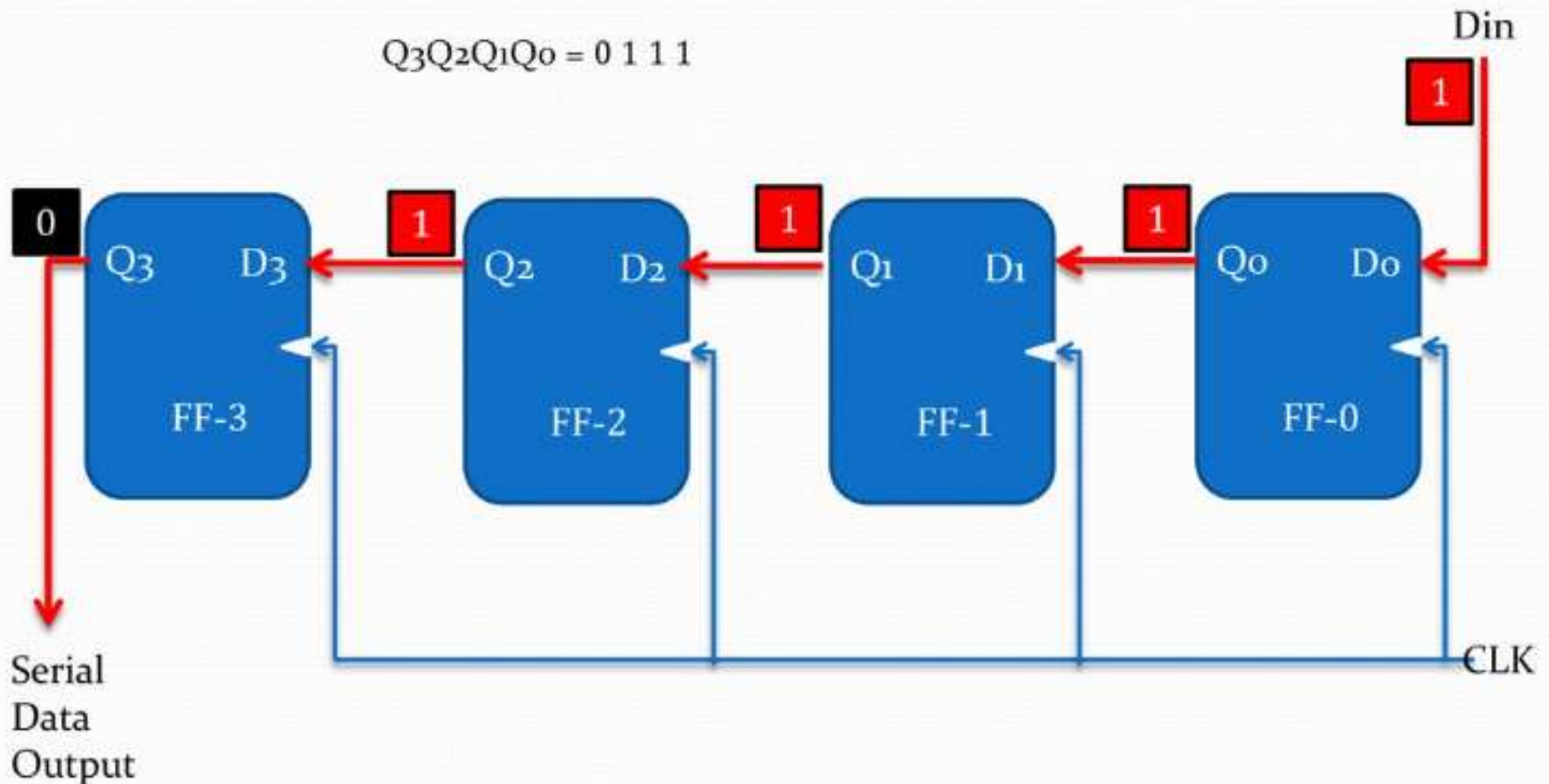

Serial input Serial Output (Shift Left Mode)


- Apply the NEXT bit to Din . So if Din =1.
- As soon as the next positive edge of the clock hits. FF- 3will SET and the stored data changes to,

$$Q_3Q_2Q_1Q_0 = 1111$$

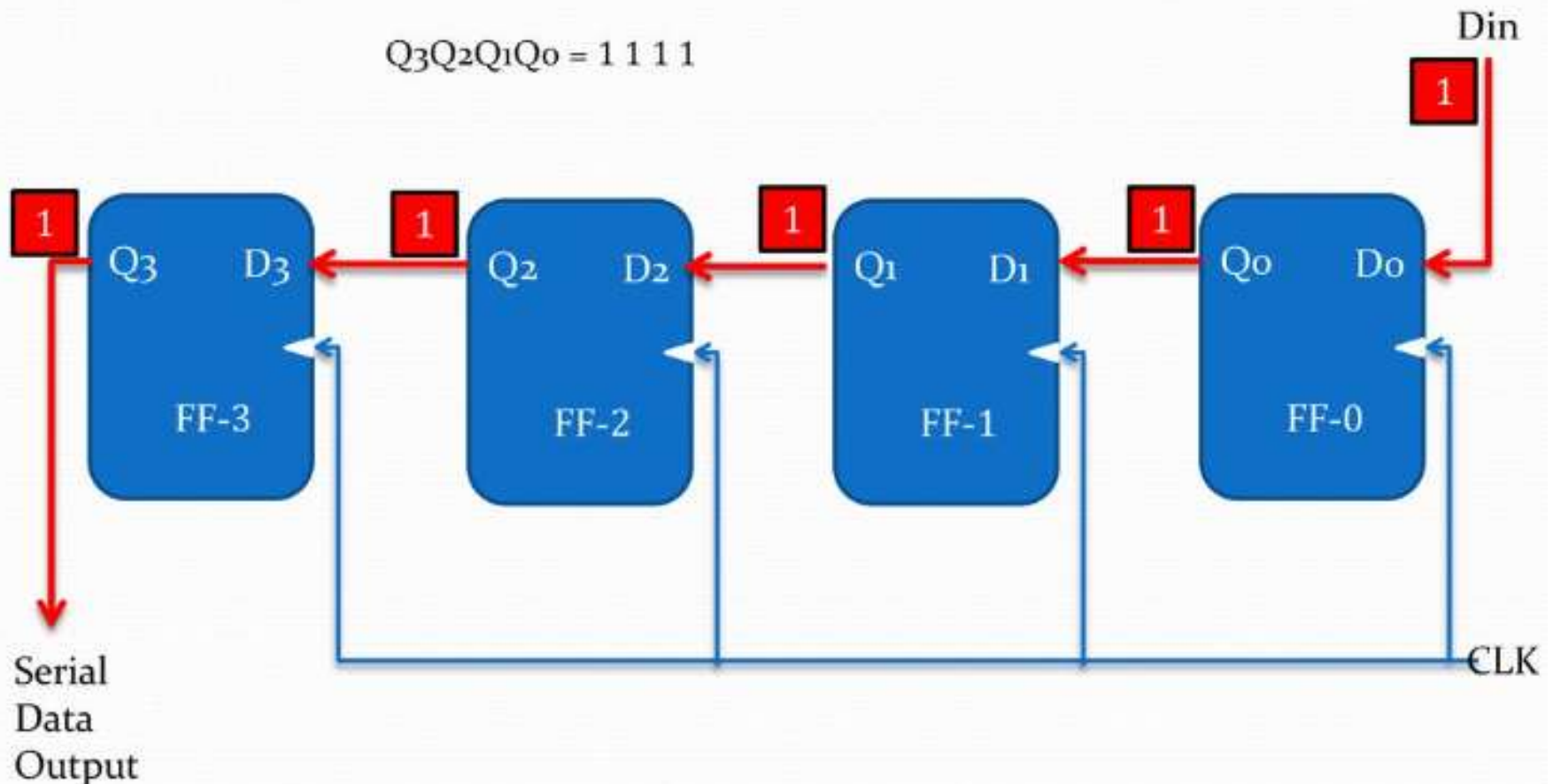


Summary of shift left operation

CLK	Q ₃	Q ₂ =D ₃	Q ₁ =D ₂	Q ₀ =D ₁	Serial input D _{in} = D ₀
	0	0	0	0	
↑	0	0	0	1	← 1
↑	0	0	1	1	← 1
↑	0	1	1	1	← 1
↑	1	1	1	1	← 1

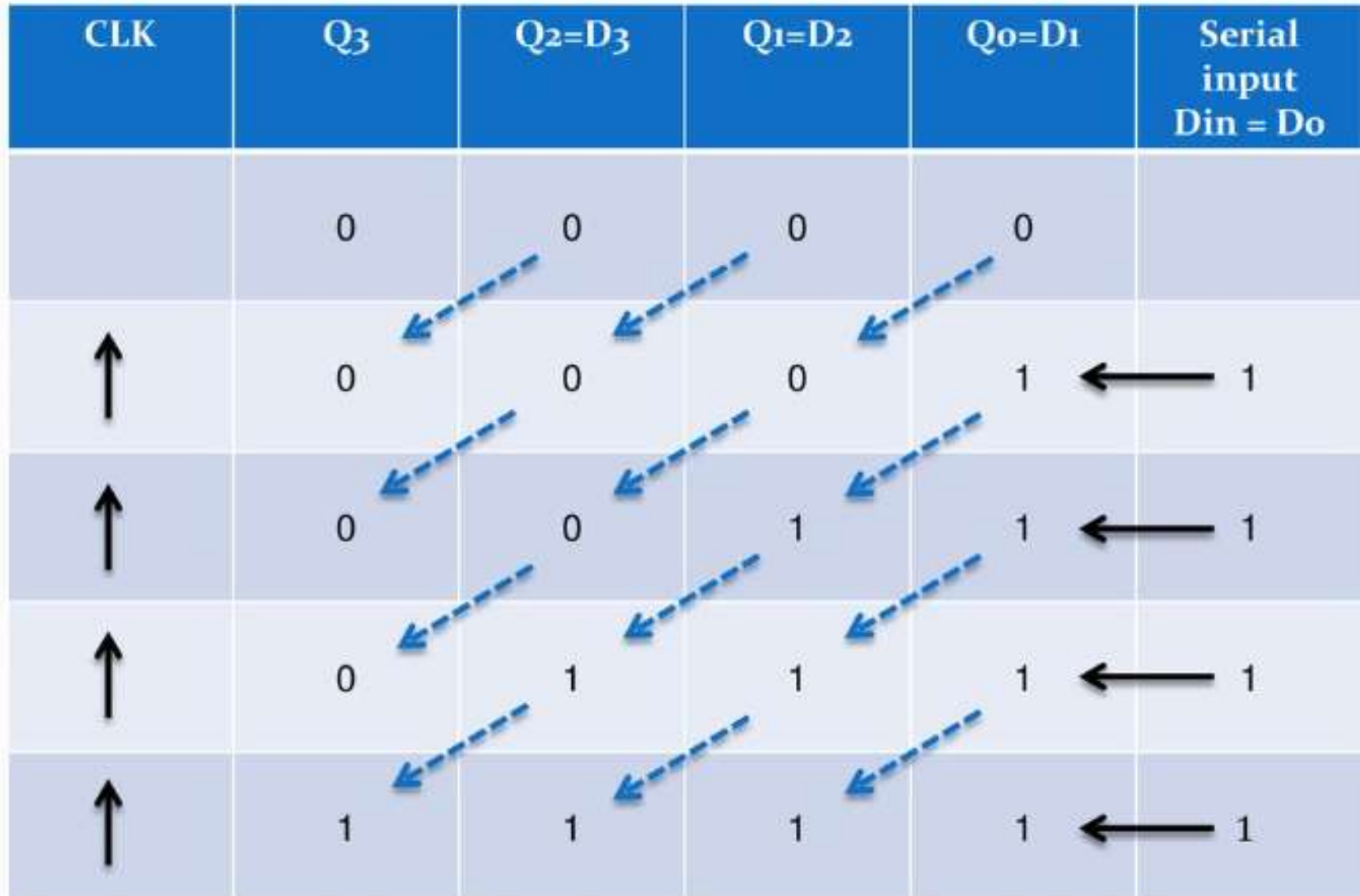


 Serial input Serial Output (Shift Right Mode)




Serial input Parallel Output (SIPO)

 - In this operation the data is entered serially and taken out in parallel.
- That means first the data is loaded bit by bit. The output are disabled as the loading is taking place.
- Number of clock cycles required to load a four bits data is 4. Hence the speed of operation of SIPO mode is same as that of SISO mode.




Parallel input Parallel Output (PIPO)

- In this operation the data are entered parallel.
- The 4-bit binary input B_0, B_1, B_2, B_3 is applied to data inputs D_0, D_1, D_2 and D_3 respectively of the four flip-flops.
- As soon as a positive clock edge is applied, the input binary bits will be loaded into the flip-flops simultaneously.
- The loaded bits will appear simultaneously to the output side. **ONLY ONE CLOCK IS ESSENTIAL TO LOAD ALL THE BITS.**

 


Parallel input Serial Output (PISO)

 - In this operation the data are entered parallel.
- Output of pervious FF is connected to the input of the next via a combinational circuit.
- The binary input data B_0, B_1, B_2, B_3 is applied through the same the combinational circuit.
- There are two modes in which this circuit can work namely **shift mode** or **load mode**.



4 bit bidirectional shift registers

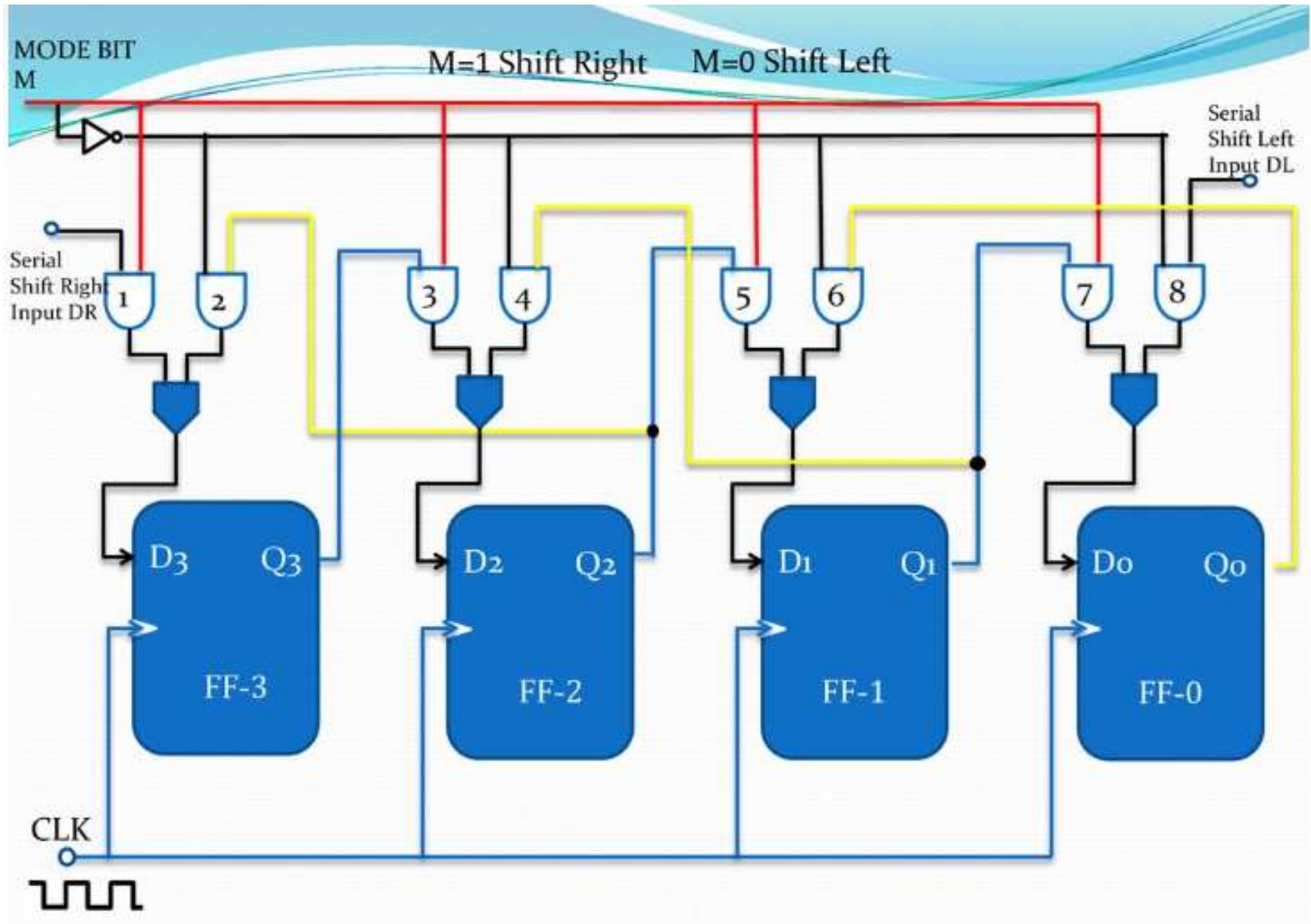

4-bits Universal Shift Register

Mode Control		Register Operation
S ₁	S ₀	
0	0	No change
0	1	Shift Right
1	0	Shift Left
1	1	Parallel load

Applications of shift Register

1. For Temporary data storage.
2. For multiplication and division
3. As a delay line
4. Ring Counter
5. Parallel to serial converter